

Pinewood Race Circuit

Track 11-7/8" total width

Lane tracks 1.5" wide

3.75" between lane edges

5/8" on each side of lane for vehicles

2.5" between max lane widths

5mm 940nm LEDs Infrared Emitter and IR Receiver

Receiving Angle: 40 degrees

Forward Voltage: 1.2-1.3V, Power: 0.15 W

Maximum power: 70 mw;

Maximum forward current: 30 ma;

Maximum reverse voltage: 5 v;

Maximum pulse current peak: 75 ma;

White: Emitter

Black: Receiver

<https://www.adafruit.com/product/3500>

https://cdn-learn.adafruit.com/assets/assets/000/049/778/original/adafruit_products_Adafruit_Trinket_M0.png

Digital #3/A3 as input

Digital #4/A4 as input


<https://www.arduino.cc/en/Tutorial/Smoothing>

5K between sensor and analog pin before ground

3.3V source from Trinket M0

4 LED's; 1.2 V @ 20 mA = 47 ohm @ 1/8 W

<http://ledcalc.com/>

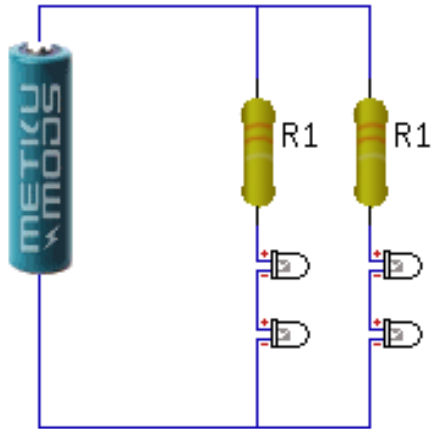

<http://www.me.umn.edu/courses/me2011/arduino/technotes/irbeam/irbeam.html>

<http://startrobotics.blogspot.com/2013/05/how-to-use-ir-led-and-photodiode-with-arduino.html>

<https://www.electronicwings.com/arduino/ir-communication-using-arduino-uno>